


Conceptual

You can use the Arduino microcontroller to turn on a transistor using a digital output pin.

- Explore the large variable resistor
- Draw a schematic and internal diagram of your potentiometer.
- Review soldering guidelines –

Basic Make

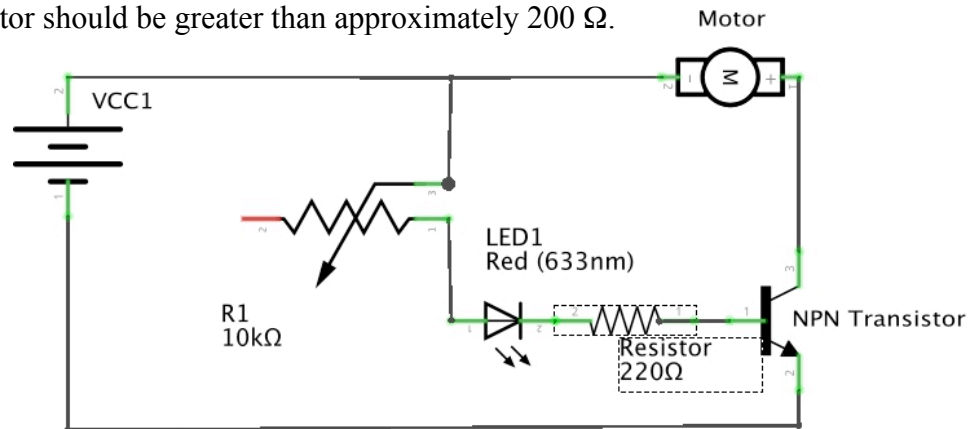- Solder breadboard pins to potentiometer (variable resistor)
- Make the circuit below
 - o Note: To avoid burning out the potentiometer the resistor should be greater than approximately 200 Ω .



fritzing

Advanced/Extended Make

- Replace variable resistor with photoresistor
- Duplicate diagrams using Fritzing

Equipment

- Computer with access to Fritzing
- Circuit components: Variable resistor

Objective

Physics Concepts

- Resistance – resistivity (material), length and cross section of wire

Experimental analysis

- Circuit design
- DMM resistance measurements

Technology Concepts

- Soldering Technique
- Schematic Symbols