

## Conceptual

You can use the Arduino microcontroller to read analog input that can be used to control an analog output.

- Read tutorial on [reading analog signals](#).
- Determine how to make a voltage divider using a variable resistor and your Arduino.
- Determine the smallest voltage that can be measured for a 5V signal that is read using 8-bit resolution. Compare to 10-bit resolution.

## Basic Make

- Design a circuit that reads an analog input and outputs an analog signal based on the input.
- Make your circuit
- Make a program to vary the load voltage from the signal measured by the analog input.
  - A useful function is “*map()*”

## Advanced/Extended Make

- Control multiple loads.
- Measure various inputs
- Explore power options:
  - USB
  - External power pack
- Duplicate diagrams using Fritzing

## Equipment

- Computer with access to Fritzing and Arduino
- Circuit components: Arduino and misc electronic parts

## Objective

Physics Concepts

- Voltage divider
- Analog to Digital
  - Resolution and bits
- Digital to Analog
  - Resolution and bits

Experimental analysis

- Circuit design – voltage divider

Technology Concepts

- Schematic Symbols
- Programming Syntax – analog read