This project asks you to create a circuit to compare binary numbers.

Construct a circuit that compares the three-bit integers $(x_2x_1x_0)_2$ and $(y_2y_1y_0)_2$, returning an output of 1 when the first of these numbers is larger and an output of 0 otherwise. Hint: You might want to look at #13 in section 11.3, which asks the same question but for two-bit integers.

MSUM MISSION: We develop knowledge, talent, and skills for a lifetime of learning, service, and citizenship.