

This project asks you to create a circuit for a light fixture controlled by four switches.

Do #8 in section 11.3.