

This project asks you to create a circuit to multiply binary numbers.

Do #14 in section 11.3.