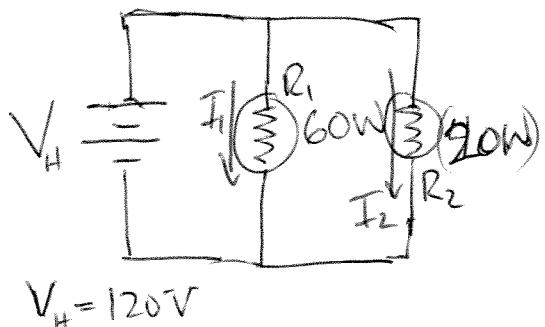



# General Problem Solving Guide

List given information, define variables, sketch picture:

PARALLEL



SERIES

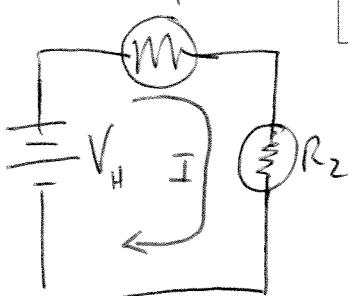

Name:	KEY
Lab Time:	
Date:	APRIL 14 2011
Test Code:	EXAM 3
Problem #:	PROBLEM 22

2 -

NOTE! HOUSEHOLD VOLTAGE IS AC  $\oplus$  NOT DC  $\frac{1}{I}$  BUT EFFECTIVELY ACTS  $\frac{1}{I}$

Simplify question, list target quantity:

1/2 WHICH LIGHT IS BRIGHTEST (USES MOST POWER) WHEN WIRED IN SERIES

List all related quantitative relationships:

$$P=VI \text{ and } V=IR \quad * \text{ASSUME LIGHTBULBS ARE RESISTORS}$$

$$2 \therefore P=\frac{V^2}{R} \quad P=I^2R$$

$$R_{\text{TOT}} = \sum_i R_i \text{ (SERIES)} \quad R_{\text{TOT}} = \left[ \sum_i \frac{1}{R_i} \right]^{-1} \text{ PARALLEL}$$

Outline approach, sketch diagrams if needed (or sketch next to pictures above):

(1) FIND RESISTANCES OF EACH BULB WHEN IN PARALLEL USING KNOWN POWER RATINGS

(2) USE BULB RESISTANCES TO FIND CURRENT AND HENCE POWER USED BY EACH BULB IN SERIES

II

Obtain a general solution:

① VOLTAGE ACROSS EACH BULB IS SAME IN PARALLEL.

$$P = \frac{V^2}{R} \quad V = 120V$$

$$R_1 = \frac{(120V)^2}{60W} = 240\Omega$$

$$R_2 = \frac{(120V)^2}{20W} = 720\Omega$$

② CURRENT THROUGH EACH RESISTOR IS THE SAME IN SERIES.

$$R_{TOT} = R_1 + R_2 = 960\Omega$$

$$\frac{V_{TOT}}{R_{TOT}} = I_{TOT} = 0.125A$$

$$P_r = I^2 R$$

$$P_1 = (0.125A)^2 \cdot 240\Omega = 3.75W$$

$$P_2 = (0.125A)^2 \cdot 720\Omega = 11.25W$$

↑  
REQUIRES MORE VOLTAGE

$$V_2 = IR_2 = 90V$$

$$\left[ \begin{array}{l} V_1 = IR_1 = 30V \\ V_{TOT} = V_1 + V_2 \end{array} \right]$$

$\sum V = 0$  around any loop

Check Units:

$$\Omega = \frac{V^2}{W} = \frac{V^2}{VA} = \frac{V}{A} = \Omega \quad \checkmark$$

$$\frac{V}{\Omega} = A \quad \checkmark$$

$$W = A^2 \Omega = A(A\Omega)^2 = AV \quad \checkmark$$

Check Limiting Cases:

①  $P \uparrow \quad R \downarrow \quad \checkmark \quad$  PATH OF LEAST RESISTANCE

II  $V \uparrow \quad R \nabla \uparrow \quad \checkmark \quad$  EASIER TO PUSH THROUGH BIG R WITH BIG V

②  $R_{TOT} \uparrow \quad I_{TOT} \downarrow \quad \checkmark$

$I \uparrow \quad P \uparrow \quad \checkmark$

$R \uparrow \quad P \uparrow \quad \checkmark$

Obtain a numeric solution:

(i.e. plug in the numbers)

PARALLEL      SERIES

II  $60W \rightarrow 3.75W$

$20W \rightarrow 11.25W \leftarrow \text{BRIGHT}$

\* Dim bulb is now the bright one.  
Why is solution reasonable? Explain.

- UNITS CHECK

- LIMITING CASES CHECK

- BIGGER RESISTANCE IN SERIES USES MORE OF THE VOLTAGE AND HENCE POWER

- BIGGER POWER USED IN PARALLEL IS PATH OF LEAST RESISTANCE (LOWEST R)