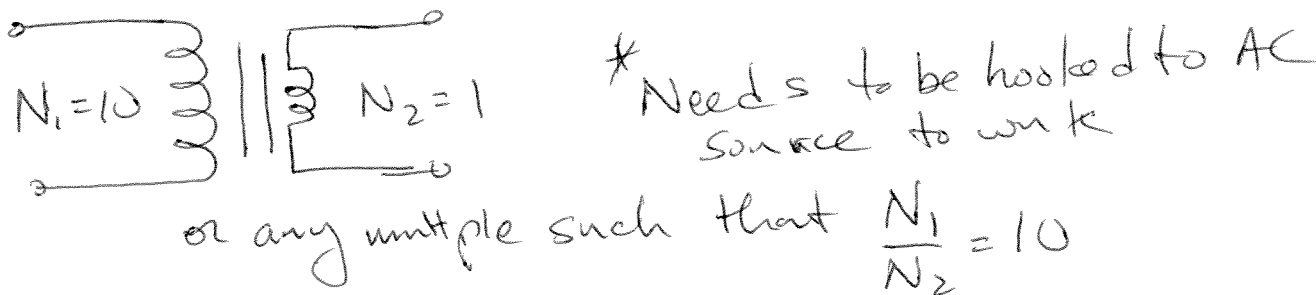


Physics 161 Quiz – Magnetic Flux and Transformers

Name KEY
 Lab Time _____


1. [2 PTS] Draw and label a picture of a 10:1 transformer.



2. [3 PTS] The transformer above is hooked to a 9 volt battery. What are the possible output voltages?

Transformers need changing flux —
 they do not work w/ DC $V_{out} = 0$

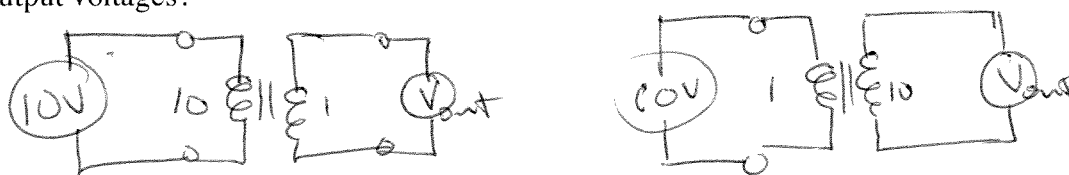3. [3 PTS] The transformer above is hooked to a 60 Hz 10 V rms function generator. What are the possible output voltages?



$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$

$$V_{out} = \left(\frac{1}{10}\right) 10V = 1V \quad \text{or} \quad V_{out} = \left(\frac{10}{1}\right) 10V = 100V$$

4. [2 PTS] The primary coil of a transformer draws 4.0 A rms current when plugged into a 120 V outlet. The secondary voltage is 40 V. What current does the secondary coil of the transformer deliver to the load?

$$P = IV$$

$$P_1 = P_2$$

$$(4A)(120V) = I_2(40V)$$

$$(4A) \cdot 3 = I_2 = \underline{12A \cdot rms}$$