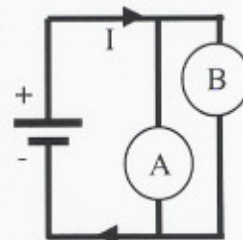


Exam 2 – Circuits


This is a closed book examination. However, you may use a 4x5 index you have created on this exam. There is extra scratch paper available. Please explain your answers. Your explanation is worth 3/4 of the points on multiple-choice questions.

- 1) [4 PTS] Two light bulbs are connected to a battery as shown in the diagram to the right. Bulb A is brighter than bulb B. What happens to the brightness when you switch the location of bulb A and bulb B?
- Bulb A is still brighter
  - Bulb B is now brighter
  - Depends on direction of current
  - Bulb B and Bulb A are now the same brightness




Current is still the same since voltage is the same  $V=iR$   
 $P=iV = \frac{V^2}{R}$  so no change

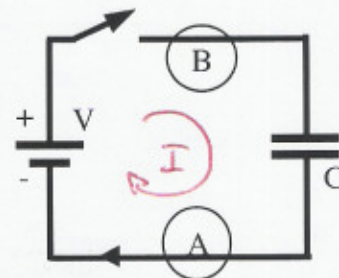- 2) [4 PTS] In the circuit to the right the capacitor is initially uncharged. If you want a light bulb to light when you throw the switch, where should you place it?
- Insert the light bulb at A.
  - Insert the light bulb at B.
  - Either position A or B will light the bulb.
  - Bulb will not light in this circuit. Neither position A or B will light the bulb.



Current will flow around entire circuit. Current is not restricted to flow on just the top or bottom

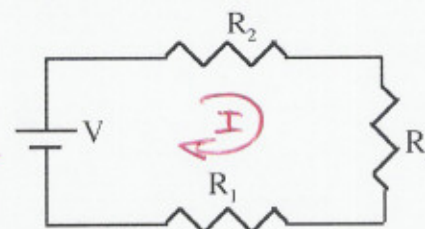- 3) [4 PTS] You connect three resistors to a battery as shown in the diagram to the right. The current through each resistor
- is the same.
  - is different.
  - is zero.
  - depends on the polarity of the battery.
  - depends on which resistor is the smallest.



In a series circuit the current has no choice - it flows through each circuit element

- 4) [4 PTS] A wire with a resistance,  $R_1$ , is replaced by a new wire that is made out of the same material and is the same length but has twice the cross-sectional radius. What is the resistance of this new wire,  $R_2$ ?

- Smaller,  $R_2 = \frac{1}{4}R_1$ .
- Smaller,  $R_1 = \frac{1}{2}R_1$ .
- The same,  $R_2 = R_1$ .
- Larger,  $R_2 = 2R_1$ .
- Larger,  $R_2 = 4R_1$ .

$R = \rho \frac{L}{A} = \frac{\rho L}{\pi r^2}$  so  $R(r) \propto \frac{1}{r^2}$


Resistance decreases -  $r_2 = 2r_1$  so

$R_2 = \frac{1}{4} R_1$

$R_2 = \frac{\rho L}{\pi (2r_1)^2} = \frac{\rho L}{4\pi r_1^2} = \frac{1}{4} R_1$

KEY

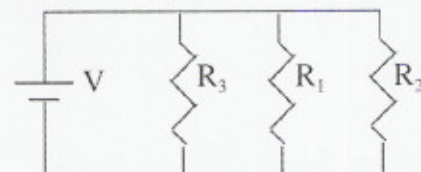- 5) [4 PTS] You connect three resistors to a battery as shown in the diagram to the right. The current through each resistor
- is the same.
  - is different.**
  - is zero.
  - depends on the polarity of the battery.
  - depends on which resistor is the smallest.



$V = IR$   
 Voltage drop across each resistor is the same...

$I = \frac{V}{R}$  so  $I(R)$

- 6) [4 PTS] For the above circuit (problem #5)  $R_1=50\Omega$ ,  $R_2=500\Omega$  and  $R_3=350\Omega$ . The voltage across  $R_1$
- is greater than the voltage across  $R_2$ .
  - is less than the voltage across  $R_3$ .
  - is less than  $V$ .
  - depends on the current through  $R_2$  and  $R_3$ .
  - is equal to  $V$ .**


Voltage drop across all resistors is the same.  
 $V_1 = V_2 = V_3 = V$

- 7) [4 PTS] For the above circuit (problem #5) what is the total resistance for the circuit?
- $R_3 > R_{total} > R_1$
  - $R_2 > R_{total} > R_3$
  - $R_{total} > R_2$
  - $R_1 > R_{total}$**
  - None of the above


$\frac{1}{R_{total}} = \sum_i \frac{1}{R_i}$

$R_{total}$  is less than the smallest resistor - you are adding more paths so resistance has to decrease.

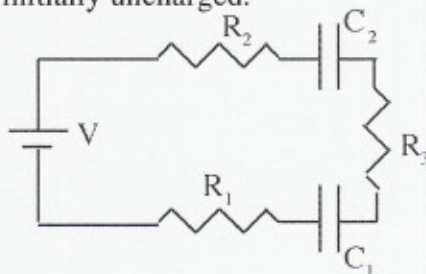
- 8) [12 PTS] You construct the following circuit with  $R_1=50\Omega$ ,  $R_2=500\Omega$ ,  $R_3=350\Omega$ ,  $C_1=400\mu F$ ,  $C_2=500\mu F$  and  $V=9V$ Volts. The capacitors are initially uncharged.
- What is the time constant?
  - Which resistor has the largest voltage drop across it?
  - Graph the voltage across  $C_2$  as a function of time.
  - Graph the voltage across  $R_3$  as a function of time.



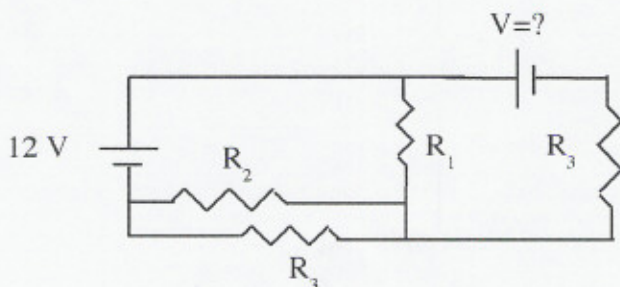
- 9) [8 PTS] Solve for the unknown source voltage and the power delivered by the unknown battery in the diagram below. The current through  $R_1$  is 1 Ampere while  $R_1 = 9\Omega$ ,  $R_2 = 3\Omega$  and  $R_3 = 1\Omega$ . NOTE: A correct setup is worth 6 PTS.



8

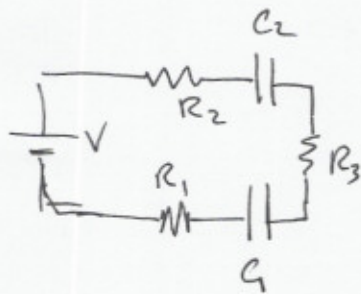

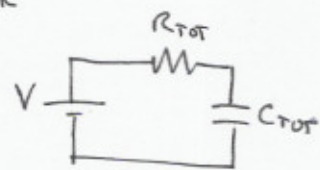$V = 9V$   
 $R_1 = 500\Omega \quad R_2 = 500\Omega \quad R_3 = 350\Omega \quad R$   
 $R_{TOT} = \sum R_i = 900\Omega$   
 $C_1 = 400\mu F \quad C_2 = 500\mu F$   
 $C_{TOT} = \left(\sum \frac{1}{C_i}\right)^{-1} = \frac{1}{4500} F \quad (222\mu F)$



[Simplify the circuit]

(a)  $\tau = RC = 900\Omega \cdot \frac{1}{4500} F = \frac{1}{5} s \quad (0.2 s)$

(b) Current is ~~constant~~ same through all the circuit elements  
 $V = IR$  so the resistor with the largest value needs the most voltage  
 $R_2 = 500\Omega$  has largest voltage drop

(c)  $Q = C_{TOT} V_C$  and  $IR_{TOT} = V_R$

Check units  
 Check  $\Sigma V$   
 Check Behavior  $t \uparrow V \uparrow V_R \downarrow I \downarrow$


$\frac{dI(t)}{dt} = \frac{dV_C(t)}{dt}$  for each capacitor  
 to find  $V_C(t)$  integrate

$V_C(t) = \int \frac{I(t)}{C_2} dt$   
 $= \frac{1}{C_2} \int I_0 e^{-t/\tau} dt$   
 $= \frac{I_0}{C_2} \int e^{-t/\tau} dt$   
 $= \frac{I_0}{C_2} \cdot -\tau e^{-t/\tau} + V_{const}$

$V(0) = 0$  so  $V_{const} = \frac{I_0 R_{TOT} C_{TOT}}{C_2}$

$V_C(t) = I_0 R_{TOT} \frac{C_{TOT}}{C_2} (1 - e^{-t/\tau})$

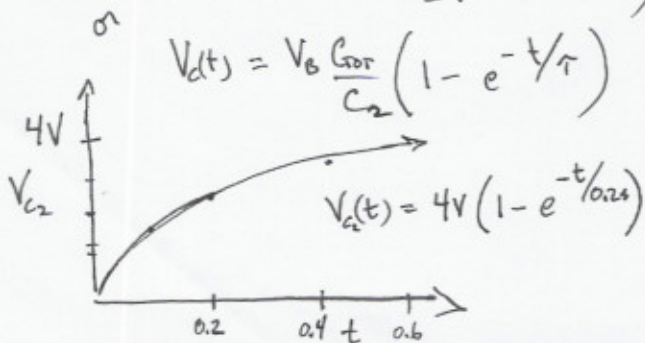
$V_C(t) = V_B \frac{C_{TOT}}{C_2} (1 - e^{-t/\tau})$



— Derivation —

$V = V_R + V_C$   
 $V = IR_{TOT} + \frac{Q}{C_{TOT}}$   
 $\frac{dV}{dt} = 0 = \frac{d}{dt} \left( IR_{TOT} + \frac{Q}{C_{TOT}} \right) = R_{TOT} \frac{dI}{dt} + \frac{1}{C_{TOT}} \frac{dQ}{dt}$   
 $0 = R_{TOT} C_{TOT} \frac{dI}{dt} + I$   
 solution is exponential function  
 $I(t) = I_0 e^{-t/RC}$   
 Initially  $V_C = 0$  so  $I_0 = \frac{V_B}{R_{TOT}} = \frac{9V}{900\Omega}$   
 $I(t) = 0.01 e^{-t/0.25}$  Amps

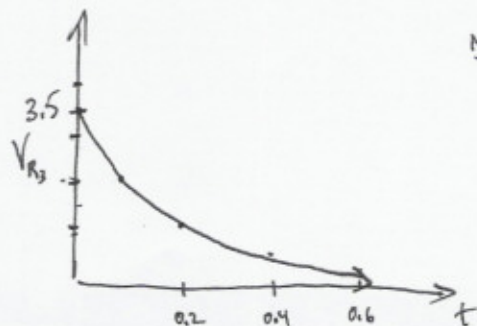(d)  $V_{R3}(t) = \frac{V_B R_3}{R_{TOT}} e^{-t/\tau} = 3.5V e^{-t/0.25}$




NOTE:  
 $V_{R3}(t) = 3.5V e^{-t/0.25}$   
 $V_{R1}(t) = 0.5V e^{-t/0.25}$   
 $V_C(t) = 5V(1 - e^{-t/0.25})$

9


EXAM 2 2007

2

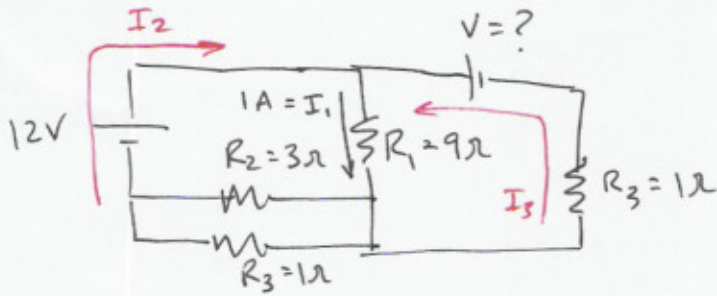

Simplify the circuit - namely  $R_2$  is parallel to  $R_3$
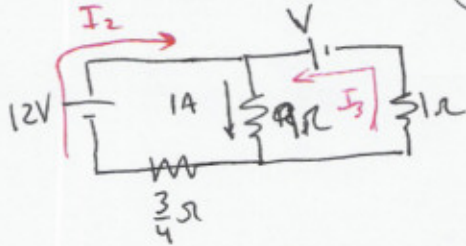
$$\cancel{3\Omega} // 1\Omega = \left( \frac{1}{3\Omega} + \frac{1}{1\Omega} \right)^{-1} = \frac{3}{4}\Omega$$



$$(1) \quad IA = I_2 + I_3$$

$$(2) \quad 12V - (IA)(9\Omega) - I_2\left(\frac{3}{4}\Omega\right) = 0$$

$$(3) \quad V - (IA)(9\Omega) - I_3(1\Omega) = 0$$

$$\Rightarrow I_2 = \frac{3V}{\frac{3}{4}\Omega} = \boxed{4A = I_2}$$

$\Rightarrow$  then from equation (1)

$$1A = 4A + I_3 \quad \boxed{I_3 = -3A}$$

I picked the wrong direction initially so this means current is being forced through the unknown battery

$\Rightarrow$  from equation (3)

$$V = 9V + (-3A)(1\Omega)$$

$$\boxed{V = 6V}$$

$$P = VI$$

$$P = (6V)(-3A)$$

$$= -18W$$

The battery is being charged!

□ check units

□ check  $\sum V = 0$

□ check  $\sum I = 0$

(Do these for your new values (w/ correct current directions))