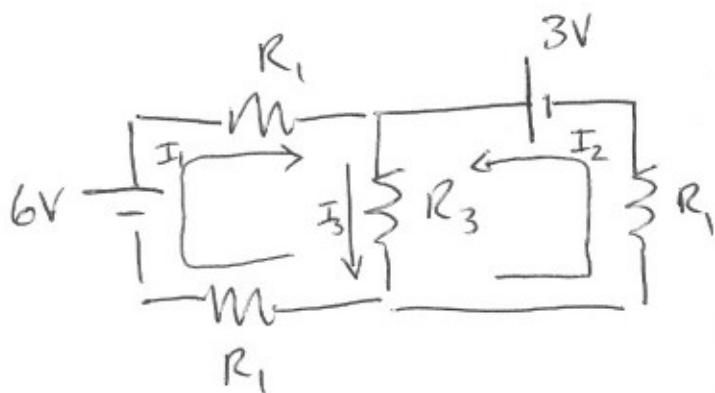


Circuits Redox



$$R_1 = 3\Omega$$

$$R_3 = 10\Omega$$

- (A) FIND POWER IN \$R_3\$
- (B) FIND POWER PROVIDED BY BOTH BATTERIES.

WANT POWER USED IN \$R_3\$:

$$I_3 = I_1 + I_2 \quad I_2 = I_3 - I_1$$

$$6V - I_1 R_1 - I_3 R_3 - I_1 R_1 = 0$$

$$3V - I_3 R_3 - I_2 R_1 = 0 = 3V - I_3 R_3 - (I_3 - I_1) R_1 = \left(\begin{array}{l} \text{substitute} \\ \text{for } I_2 \end{array} \right)$$

$$6V - I_1 (2 \cdot 3\Omega) - I_3 10\Omega = 0$$

$$\frac{6V - I_3 10\Omega}{6\Omega} = I_1$$

solve for \$I_1\$ and substitute in

$$3V - I_3 10\Omega - I_3 3\Omega + I_1 3\Omega = 0$$

$$3V - I_3 13\Omega + 3\Omega \left(\frac{6V - I_3 10\Omega}{6\Omega} \right) = 0 \quad \text{solve for } I_3$$

$$3V - I_3 13\Omega + 3V - I_3 5\Omega = 0 = 6V - I_3 18\Omega$$

$$I_3 = \frac{6V}{18\Omega} = \frac{1}{3} A$$

$$P_3 = I_3 V_3 = I_3 (I_3 R_3) = I_3^2 R_3$$

$$P_3 = \left(\frac{1}{3} A \right)^2 \cdot 10\Omega = 1.11 W = \frac{10}{9} W$$

Find I_1 and I_2

$$I_1 = \frac{6V - I_3 \cdot 10\Omega}{6\Omega} = 1A - \frac{1}{3}A \cdot \frac{10\Omega}{6\Omega} = \frac{8}{18}A = \boxed{\frac{4}{9}A = 0.44A = I_1}$$

$$I_2 = I_3 - I_1 = \frac{1}{3}A - \frac{4}{9}A = \boxed{-\frac{1}{9}A = -0.11A = I_2}$$

so I_2 is "charging" the 3V battery.

$$P_{6V} = I_1 V_6 = \frac{4}{9}A \cdot 6V = \boxed{2.66W = \frac{8}{3}W}$$

$$P_{3V} = I_2 V_3 = -\frac{1}{9}A \cdot 3V = \boxed{-0.33W = -\frac{1}{3}W}$$

Check Power $P_{6V} + P_{3V} + P_{R_3} + \sum P_{R_i} = 0$

$$\frac{8}{3}W + (-\frac{1}{3}W) + (-\frac{10}{9}W) + 1.22W = 0 \quad \checkmark$$

(2.66) (-.33) (-1.11) (-1.22)

$$\begin{aligned} \sum P_{R_i} &= 3\Omega \left(\frac{4}{9}A\right)^2 \cdot 2 \\ &\quad + 3\Omega \left(\frac{1}{9}A\right)^2 \\ &= 1.22W \end{aligned}$$

Check I_2 from $\Delta V = 0$ equation

$$3V - I_3 R_3 - I_2 R_1 = 0$$

$$I_2 = \frac{3V - \frac{1}{3}A \cdot 10\Omega}{3\Omega} = 1A - \frac{10}{9}A = -\frac{1}{9}A \quad \checkmark$$

Check units — \checkmark