

Exam 2 – Capacitance, Circuits and Magnetism

March 5, 2009


This is a closed book examination. However, you may use a 8.5" x 11" sheet of paper with your own notes during this exam. There is extra scratch paper available. Please explain your answers. Your explanation is worth 3/4 of the points on multiple-choice questions.

- 1) [4 PTS] What is the net force on a neutron ($q = 0$) with velocity $\vec{v} = 50\text{m/s } \hat{i}$ traveling through a region of space with $\vec{E} = 40\text{V/m } \hat{j}$ and $\vec{B} = 1.5\text{T } \hat{k}$?

$$\vec{F} = q(\vec{E} + \vec{v} \times \vec{B}) \quad q = 0 \quad \therefore \vec{F}_{\text{NET}} = 0$$

- 2) [4 PTS] Two light bulbs (A and B) are connected in series. Bulb A is twice as bright as bulb B. What must be true?

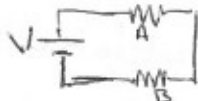- a) $2R_B = R_A$
- b) $\sqrt{2} I_B = I_A$
- c) Bulb A receives the current from the battery first (closest to positive terminal)
- d) Bulb B receives the current from the battery first (closest to positive terminal)
- e) $2R_A = R_B$
- f) $\sqrt{2} I_A = I_B$



$$P_A = 2P_B \quad I_A = I_B$$

$$P = IV = I^2 R$$


$$V = IR$$

$$I_A^2 R_A = 2 I_B^2 R_B$$

$$I^2 R_A = 2 I^2 R_B \quad \therefore R_A = 2R_B$$

- 3) [4 PTS] You connect three resistors to a battery as shown in the diagram to the right. Which resistor has the most current flowing through it?

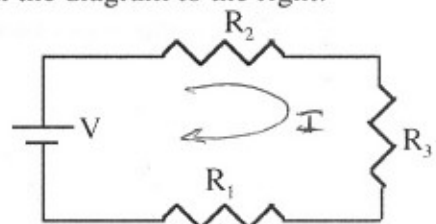- a) R_1
- b) R_2
- c) R_3
- d) Which ever one has the smallest resistance.
- e) Which ever one has the largest resistance.
- f) The current is the same through all of them.



Current is constant through objects in series -
* current in is equal to current out

- 4) [4 PTS] You are measuring the voltage across a capacitor with a charge Q on it. How does the energy change when you insert a dielectric with $\kappa=2$ into the capacitor.

- a) The energy decreases.
- b) The energy does not change.
- c) The energy increases.

$$C = \frac{Q}{V} \quad V = \frac{Q}{C} \quad C_0 = \frac{\epsilon_0 A}{d}$$

$$U = \frac{1}{2} QV = \frac{1}{2} \frac{Q^2}{C}$$


$$U_0 = \frac{1}{2} \frac{Q^2}{\epsilon_0 A}$$

$$U_1 = \frac{1}{2} \frac{Q^2}{\kappa \epsilon_0 A}$$


Charge is constant
Capacitance will change

$$\therefore U_1 = \frac{1}{\kappa} U_0$$

Voltage changes

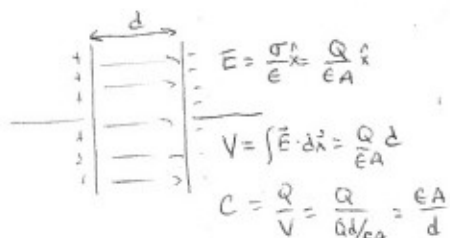

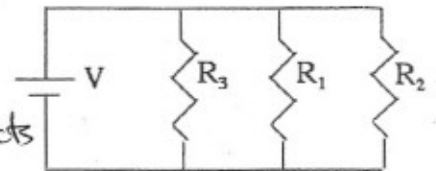- 5) [4 PTS] The light bulbs in the circuit to the right have different resistances, $R_1 = 2R_2 = 4R_3$. Which bulb is brightest (uses the most power)?



- a) R_1
 b) R_2
 c) R_3
 d) All the light bulbs are of equal brightness since they have the same voltage across them.

Voltage is same across objects in parallel
 $P = IV = V^2/R$


\therefore Bulb with lowest R has greatest power -
 $R_3 < R_2 < R_1$

- 6) [4 PTS] A charged particle is moving in a uniform magnetic field (coming out of the page) as shown in the figure to the right. What type of particle would follow the path indicated?

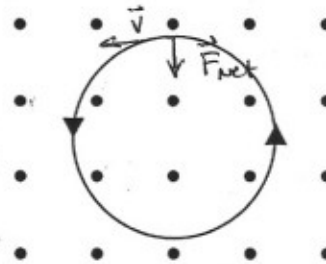- a) Proton
 b) Neutron
 c) Electron
 d) Photon

$$\vec{F} = q \vec{v} \times \vec{B}$$

For circular motion you need a central force (acceleration)



$\vec{v} \times \vec{B}$ gives a force radially outward...
 so charge needs to be negative


Note A positive charge would go in a CW direction


- 7) [12 PTS] A charged capacitor ($C = 3.2 \text{ mF}$) is connected to a resistive load ($R = 100 \Omega$) at time $t = 0 \text{ s}$. The capacitor is initially charged to 5.1 Volts.

- a) What is the time constant for this circuit? $\tau = RC = (100 \Omega)(3.2 \text{ mF}) = 0.32 \text{ s}$
 b) What is the initial energy stored in the capacitor? $U = \frac{1}{2} QV = \frac{1}{2} (CV)V = \frac{1}{2} CV^2 = \frac{1}{2} (3.2 \text{ mF})(5.1 \text{ V})^2$
 c) How much energy is left in the capacitor at time $t = \tau$?
 d) What is the power used by the load as a function of time?

- 8) [12 PTS] Solve for the unknown source voltage, the current through resistor R_1 and the power used by resistor R_5 in the diagram below. The current through R_2 is 1,666 mA while $R_1 = 8 \Omega$, $R_2 = R_5 = 2 \Omega$ and $R_3 = 4 \Omega$.

NOT IN CIRCLED

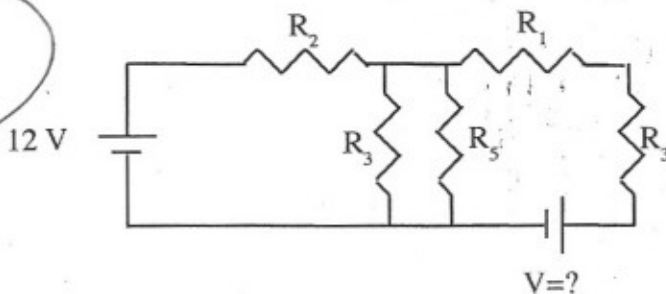

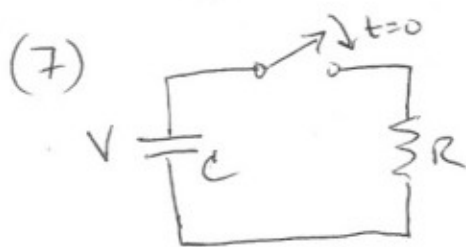

$$V_0 = 5.1 \text{ V}$$

$$C = 3.2 \text{ mF}$$

$$R = 100 \Omega$$

(a) $\tau = RC = (100 \Omega)(3.2 \text{ mF}) = 0.32 \text{ s}$

(b) $U_0 = \frac{1}{2} QV = \frac{1}{2} (CV)V = \frac{1}{2} CV^2 = \frac{1}{2} (3.2 \text{ mF})(5.1)^2 = 0.042 \text{ J} \text{ (42 mJ)}$

(c) The voltage (and current) follow an exponential decay

$$V(t) = V_0 e^{-t/\tau} \quad I(t) = C \frac{dV(t)}{dt} = CV_0 \frac{d}{dt} e^{-t/\tau} = CV_0 \left(-\frac{1}{\tau}\right) e^{-t/\tau}$$

$$I(t) = -\frac{V_0}{R} e^{-t/\tau}$$

$$P(t) = V(t)I(t) = -\frac{V_0^2}{R} e^{-t/\tau} \cdot e^{-t/\tau} = -\frac{V_0^2}{R} e^{-2t/\tau}$$

Power is negative since energy is leaving -

$$U(t) = \int_0^t P(t) dt = -\frac{V_0^2}{R} \int_0^t e^{-2t/\tau} dt = +\frac{\tau}{2} \frac{V_0^2}{R} e^{-2t/\tau} + \text{constant} = \frac{1}{2} CV_0^2 e^{-2t/\tau} + \text{const.}$$

Find constant by noting $U(0) = \frac{1}{2} CV_0^2$ [from (b) above]
 \therefore constant is 0

$$U(t) = \frac{1}{2} CV_0^2 e^{-2t/\tau} \quad t = \tau$$

$$U(\tau) = \frac{1}{2} CV_0^2 e^{-2} \quad \text{so at time } t = \tau \quad U(\tau) = \frac{U_0}{e^2} = 0.0057 \text{ J} \text{ (5.7 mJ)}$$


(d) From above

$$P(t) = -\frac{V_0^2}{R} e^{-2t/\tau} \quad \text{leaving capacitor so } P(t) \text{ ~~from~~ used by load is (-)}$$

$$\text{LOAD } P(t) = \frac{V_0^2}{R} e^{-2t/\tau} = 0.26 e^{-2t/\tau} \text{ W}$$

$$= 0.26 e^{-t/1.6} \text{ W}$$

(8)

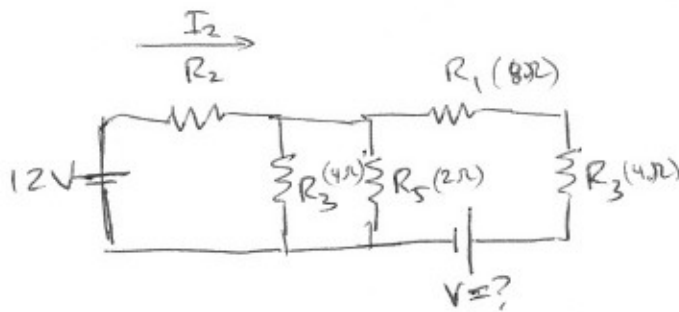

$$I_2 = 1.666 \text{ A}$$


$$R_1 = 8 \Omega$$

$$R_2 = R_5 = 2 \Omega$$

$$R_3 = 4 \Omega$$

NOTE $R_5 // R_3 \Rightarrow \left[\frac{1}{R_5} + \frac{1}{R_3} \right]^{-1} = \left[\frac{1}{4} + \frac{1}{2} \right]^{-1} = \frac{4}{3} \Omega$

Simplify the circuit

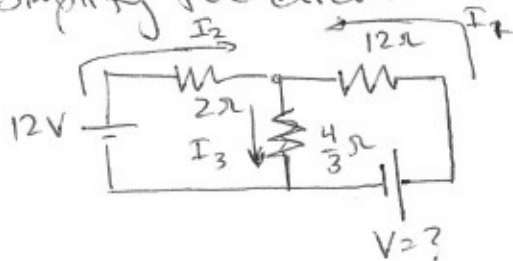

(A) $I_2 + I_1 = I_3$ current in equals current out
 $\Delta V = 0$ voltage around loop is zero

(B) $12\text{V} - I_2(2\Omega) - I_3\left(\frac{4}{3}\Omega\right) = 0$

(C) $V - I_1(12\Omega) - I_3\left(\frac{4}{3}\Omega\right) = 0$

From (B) $\frac{12\text{V} - (1.666\text{A})(2\Omega)}{\frac{4}{3}\Omega} = I_3 = \frac{13}{2} \text{ A} \quad (6.5 \text{ A})$

From (A) $I_1 = I_3 - I_2 = \frac{13}{2} \text{ A} - \frac{5}{3} \text{ A} = \frac{29}{6} \text{ A} \quad (4.83 \text{ A})$

From (C) $V = (12\Omega)\left(\frac{29}{6} \text{ A}\right) + \left(\frac{4}{3}\Omega\right)\left(\frac{13}{2} \text{ A}\right) = 58\text{V} + \frac{26}{3}\text{V} = 66.6 \text{ V}$

Power through R_5 $P_{R_5} = IV = \frac{V^2}{R}$

$$P_{R_5} = \frac{\left(\frac{26}{3}\text{V}\right)^2}{2\Omega} = 37.6 \text{ W}$$

Use voltage since current through $R_3 // R_5$ is not same but voltage is the same

$$V = \left(\frac{4}{3}\Omega\right)\left(\frac{13}{2} \text{ A}\right) = \frac{26}{3} \text{ V}$$