

Exam 2 – Capacitance, Circuits and Magnetism

March 11, 2010


This is a closed book examination but during the exam you may refer to a 4"x6" note card with words of wisdom you have written on it. There is extra scratch paper available. Please explain your answers. Your explanation is worth 3/4 of the points on all questions.

A general reminder about problem solving:

- | | |
|--|--|
| <ul style="list-style-type: none"> • Focus <ul style="list-style-type: none"> ○ Draw a picture of the problem ○ What is the question? What do you want to know? ○ List known and unknown quantities ○ List assumptions • Physics <ul style="list-style-type: none"> ○ Determine approach – What physics principles will you use? ○ Pick a coordinate system ○ Simplify picture to a schematic (if needed) • Plan <ul style="list-style-type: none"> ○ Divide problem into sub-problems | <ul style="list-style-type: none"> ○ Modify schematic and coordinate system (if needed) ○ Write general equations • Execute <ul style="list-style-type: none"> ○ Write equations with variables ○ Do you have sufficient equations to determine your unknowns? ○ Simplify and solve • Evaluate <ul style="list-style-type: none"> ○ Check units ○ Why is answer reasonable? ○ Check limiting cases! • Show All Your Work! |
|--|--|

1) [4 PTS] You connect three light bulbs (resistors) to a battery as shown in the diagram to the right. If the light bulb labeled R_2 is brightest, what must be true?

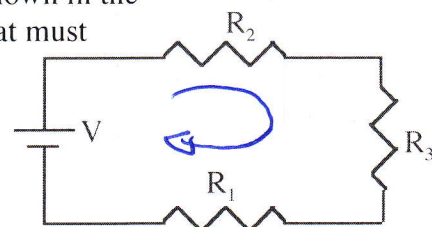- a) R_2 has the largest resistance.
- b) R_2 is first resistor so it has largest current through it.
- c) R_2 has the smallest resistance.
- d) R_2 has the smallest voltage drop.




The current is the same through all objects that are in series.

Brightness = Power = $VI = I^2R$ so largest R is brightest (since $V \approx IR$)

2) [4 PTS] A current carrying wire is placed between the poles of a strong magnet. The magnetic field is in the $-y$ direction and the wire is along the x -axis. If the wire is deflected in the $+z$ direction what is the direction of the current?

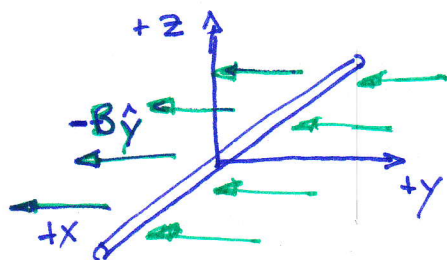- a) The current is traveling in the $-x$ direction.
- b) The current is traveling in the $+x$ direction.
- c) The current is not moving but there is a net negative charge on the wire.
- d) The current is not moving but there is a net positive charge on the wire.




$$\vec{F} = q\vec{v} \times \vec{B} = I\vec{\ell} \times \vec{B}$$

$$F_z = I I_x \times B_y$$


Current must be in $-\hat{x}$ direction

Right Rule
 $\hat{x} \times \hat{y} = \hat{z}$

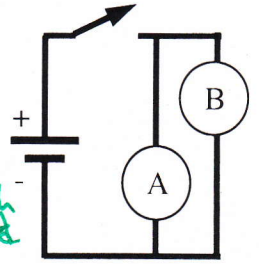The next two problems involve the circuit to the right. A capacitor is placed at position B and a light bulb is placed at position A. Assume the voltage source can provide any current.



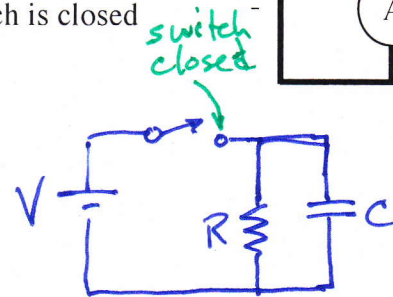- 3) [4 PTS] The capacitor is initially uncharged. When the switch is closed what happens?
- The light bulb does not light.
 - The light bulb starts off dim and then gets brighter.
 - The light bulb turns on and is a constant brightness.
 - The light bulb starts off bright and then gets dimmer.




If voltage source can supply the needed current then I is constant through resistor $I = \frac{V}{R}$

NOTE: The current diminishes through the capacitor as it charges (but doesn't affect light bulb)

- 4) [4 PTS] After a long time the switch is then opened. What happens?
- Nothing. The light bulb was off and it stays off.
 - The light bulb starts off dim and then gets brighter.
 - Nothing. The light bulb turns on and stays on.
 - The light bulb starts off bright and then gets dimmer.

Battery disconnected

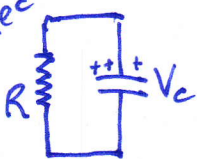

Capacitor charge (voltage) ~~and~~ creates current through resistor

$$V_R = V_C = V_0 e^{-t/\tau} \quad \tau = RC$$

- 5) [4 PTS] You are measuring the voltage across a capacitor with a charge Q on it. How does the voltage change when you insert a dielectric with $\kappa=2$ into the capacitor.

- The voltage decreases.
- The voltage does not change.
- The voltage increases.

$$Q = C_0 V$$

$$C = \frac{\kappa \epsilon_0 A}{d}$$

For parallel plate capacitor

The charge is constant so if capacitance changes the voltage will change.

$\kappa=1$ for air so $C = 2C_0$ since C increase V decreases
 ($C_0 = \frac{\epsilon_0 A}{d}$)

NOTE: for a given breakdown voltage you can store more charge

- [4 PTS] A parallel plate capacitor is charged and stores a total energy of U_i . You decide to increase the plate separation by 4 (i.e. they were separated by 1 mm and now they are separated by 4 mm). What is the new energy stored in the capacitor?

- $U_f = \frac{1}{2} U_i$
- $U_f = \frac{1}{4} U_i$
- $U_f = U_i$
- $U_f = 2 U_i$
- $U_f = 4 U_i$
- $U_f = 16 U_i$

$$U = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C}$$

$$C = \frac{1}{4} C_0$$

$$U_0 = \frac{1}{2} \frac{Q_0^2}{C_0}$$

$$U_f = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{Q_0^2}{(\frac{1}{4} C_0)} = 4 \left(\frac{1}{2} \frac{Q_0^2}{C_0} \right)$$


$$Q = Q_0$$

$$U_f = 4 U_0$$

It took energy to pull plates further apart

$E_2 A = \frac{Q A}{\epsilon}$ $E_1 = \frac{\sigma}{2\epsilon}$
 for two plates with fields $E = \frac{\sigma}{\epsilon}$
 $V = \int E \cdot dr$ $\frac{V}{d} = \frac{Q}{\epsilon A}$
 $C = \frac{Q}{V} = \frac{\epsilon A}{d}$

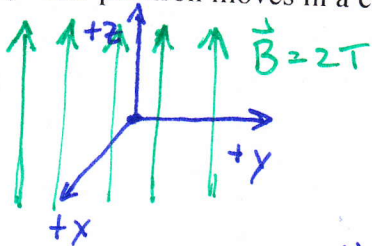- 7) [4 PTS] The radioactive decay of ^{18}F produces a positron that is initially at rest in a vacuum chamber. The positron (a positively charged electron) is in the middle of a uniform magnetic field of magnitude 2 Teslas. The field is in the $+z$ direction where the gravitational acceleration is in the $-z$ direction. How does the positron move?
- The positron moves in a circle with an angular velocity vector in the $+z$ direction.
 - (b)** The positron moves in the $-z$ direction.
 - The positron moves in the $+z$ direction.
 - The positron moves in a circle with an angular velocity vector in the $-z$ direction.




$$\vec{F} = q\vec{v} \times \vec{B} \quad \vec{F} = mg$$

$v = 0$ so the positron has no force due to \vec{B} but will move due to gravity

Note: $\vec{v}_z \times \vec{B} = 0$ so F_m will stay 0

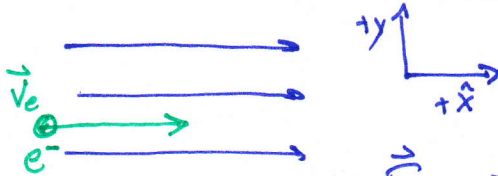- 8) [4 PTS] An electron moving in the $+x$ direction enters a region of uniform magnetic field that is also oriented in the $+x$ direction. In which direction does the electron feel a force?
- The $+y$ direction.
 - The $+z$ direction.
 - The $-y$ direction.
 - The $-z$ direction.
 - (e)** None of the above.




$$\vec{F} = q\vec{v} \times \vec{B} = 0$$

$$|F| = q|v||B|\sin\theta$$

Cross product for two parallel vectors is zero.

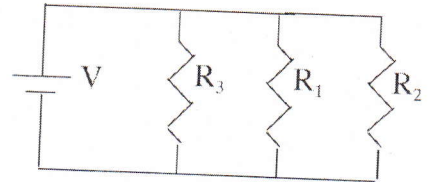- 9) [4 PTS] For the circuit to the right the light bulb labeled R_3 is the brightest and the light bulb labeled R_1 is the dimmest. The circuit is now changed to resemble the circuit in question #1. How does the brightness of the light bulbs change?
- R_2 is now the brightest light bulb.
 - R_3 is still the brightest light bulb.
 - (c)** R_1 is now the brightest light bulb.
 - All the light bulbs are of equal brightness.



Power = Brightness

$$P = VI = \frac{V^2}{R} \quad \text{since } V = IR \quad \text{Brightest will have smallest Resistance}$$


$$P_3 > P_2 > P_1 \quad \# \text{ Voltages are all the same since they are in parallel}$$

$$R_3 < R_2 < R_1$$

Now switch so resistors are in series current is the same so


$$P = I^2 R \quad P_3 < P_2 < P_1$$

Brightest was dimmest!

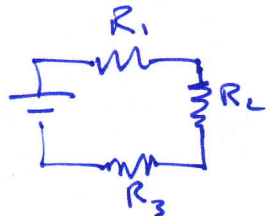

In parallel

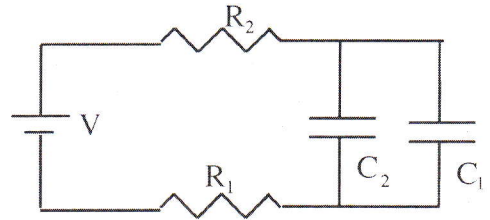10) [24 PTS] You construct the circuit shown to the right with $R_1 = 250\Omega$, $R_2 = 750\Omega$, $C_1 = 40\mu\text{F}$, $C_2 = 10\mu\text{F}$ and $V = 3\text{Volts}$. The capacitors are initially uncharged. NOTE: When graphing $V(t)$ and $I(t)$ make sure to label both axis with actual values.



- What is the time constant for the entire circuit?
- Which resistor has the largest voltage drop across it?
- Which resistor has the largest current through it?
- Graph the voltage across C_2 as a function of time.
- Graph the current through C_1 as a function of time.
- Graph the current through R_1 as a function of time.
- How long does it take C_1 to charge to 2 volts?
- What is the charge on each capacitor at $t = 75\text{ msec}$?

$$Q_1 = 93.2 \mu\text{C}$$

$$Q_2 = 23.3 \mu\text{C}$$

$$\tau = RC$$

$$R_{TOT} = R_1 + R_2 = 250 \Omega + 750 \Omega = 1 \text{ k}\Omega$$

$$C_{TOT} = C_1 + C_2 = 40 \mu\text{F} + 10 \mu\text{F} = 50 \mu\text{F}$$

$$RC = 1 \times 10^3 \Omega \cdot 50 \times 10^{-6} \text{ F} = 50 \times 10^{-3} \text{ s}$$

$$\tau = 50 \text{ msec}$$

(b) In series I is constant (same)

$$V = IR \text{ so } R_2 > R_1 \text{ and } V_2 > V_1$$

R_2 has greatest voltage drop


(c) I is the same through both resistors
Since they are in series

(d) $V_{C2} = V_{C1}$ since they are in parallel

$$V(t) = V_0 (1 - e^{-t/\tau})$$

$$V_0 = 3 \text{ Volts}$$

$$\tau = 50 \text{ msec}$$

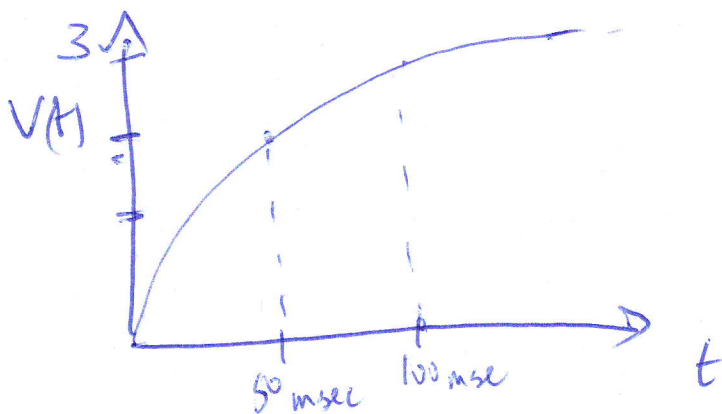

h

$$Q = CV$$

$$Q_1 = C_1 V (1 - e^{-t/\tau})$$


$$Q_2 = C_2 V (1 - e^{-t/\tau})$$

$$\frac{1}{\tau} = \ln 3 \text{ so } t = 50 \text{ msec} \cdot (\ln 3) = 54.9 \text{ msec}$$

$$3V e^{-t/\tau} = 1V \text{ so } e^{-t/\tau} = \frac{1}{3} \text{ and } \ln(e^{-t/\tau}) = \ln \frac{1}{3}$$

g
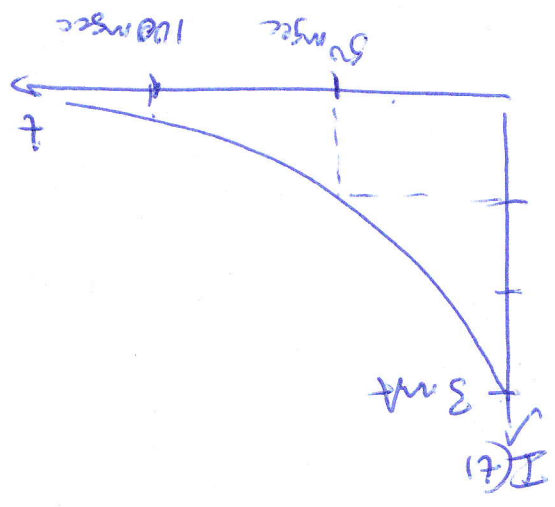
$$2 \text{ volts} = 3 \text{ volts} (1 - e^{-t/\tau})$$




$$I(t) = \frac{V_0}{R_{tot}} e^{-t/\tau} = 3 \text{ mA} e^{-t/\tau}$$

$$\Delta V(t) = V_0 - V(t) = V_0 e^{-t/\tau}$$

$$V = IR \text{ so } I_{\text{initial}} = \frac{V_{\text{tot}}}{R_{\text{tot}}}$$

f

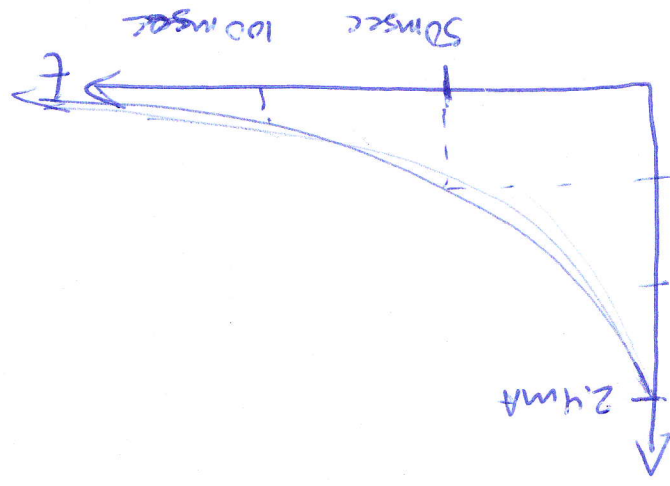

$$I_1(t) = 2.4 \text{ mA} e^{-t/\tau}$$

$$= \frac{V_0}{C_1} \cdot \frac{C_1}{R_{tot}(C_1 + C_2)} e^{-t/\tau} = \frac{3V}{3k\Omega \cdot \frac{5}{4}} e^{-t/\tau}$$

$$I_1(t) = C_1 \cdot \frac{dV(t)}{dt} = C_1 V_0 \left(-\frac{1}{\tau}\right) e^{-t/\tau}$$

e

$$Q = CV \text{ so } I = \frac{dQ}{dt} = C \frac{dV}{dt}$$