

Exam 2 – Electrodynamics

43

April 19, 2010

This is a closed book examination but during the exam you may refer to a 4"x6" note card with words of wisdom you have written on it. There is extra scratch paper available. Please explain your answers. Your explanation is worth 3/4 of the points on all questions.

A general reminder about problem solving:

- | | |
|--|--|
| <ul style="list-style-type: none"> • Focus <ul style="list-style-type: none"> ○ Draw a picture of the problem ○ What is the question? What do you want to know? ○ List known and unknown quantities ○ List assumptions • Physics <ul style="list-style-type: none"> ○ Determine approach – What physics principles will you use? ○ Pick a coordinate system ○ Simplify picture to a schematic (if needed) • Plan <ul style="list-style-type: none"> ○ Divide problem into sub-problems | <ul style="list-style-type: none"> ○ Modify schematic and coordinate system (if needed) ○ Write general equations • Execute <ul style="list-style-type: none"> ○ Write equations with variables ○ Do you have sufficient equations to determine your unknowns? ○ Simplify and solve • Evaluate <ul style="list-style-type: none"> ○ Check units ○ Why is answer reasonable? ○ Check limiting cases! • Show All Your Work! |
|--|--|

1) [4 PTS] A generator with an effective (rms) voltage of 1.5 V is connected to a transformer on a side with 1000 windings. The other side has only 10 windings so the effective (rms) output voltage is

- a) 150 V
- b) 15 V
- c) 0 V
- d) 150 mV
- e) 15 mV

$$V_{emf} = -N \frac{d\Phi}{dt} \quad \text{so} \quad \frac{V_1}{N_1} = \frac{V_2}{N_2}$$

$$\frac{1.5V}{1000} = \frac{V_2}{10}$$

$$\frac{15V}{1000} = V_2$$

$$15mV = V_2$$

↑
Need an AC voltage

2) [4 PTS] A closed loop is placed next to a wire. The wire carries an rms current of 50 mA. The loop does not move relative to the wire.

- a) There will be no induced current.
- b) There will only be an induced current if the loop moves parallel to the wire.
- c) There will only be an induced current if the loop is rotated 90° so its surface normal vector is parallel to the wire.
- d) There is a constant induced current.
- e) There is an oscillating induced current.
- f) None of the above

B field wraps around the wire

B x I so since I(t) oscillates the magnetic field oscillates.

$\Phi_m = \int B \cdot dA$ and $\frac{d\Phi_m}{dt} \neq 0 \Rightarrow$ at times (+) and then (-) so induced emf (voltage) will oscillate



3) [4PTS] When the effective (rms) voltage and current in an ac circuit are in-phase, we know

- a) the capacitive reactance is zero \times
- b) the inductive reactance is zero \times
- c) the impedance is zero \times
- d) the total reactance is $\frac{1}{2}$ of the resistance \times
- e) the circuit is being operated at its resonant frequency
- f) both (a) and (b) \times
- g) both (c) and (e) \times

when $\omega = \omega_0$ $Z = R$
 $X = 0$


In phase means the circuit is operating at resonant frequency ($S=0$)

$$\omega_0 = \frac{1}{(LC)^{1/2}} \quad Z = (R^2 + X^2)^{1/2}$$

$$S = 0 = \tan^{-1} \frac{X}{R} \quad \text{so } X = X_L - X_C = 0$$

4) [4PTS] An inductor, capacitor and resistor are connected in series to an AC voltage source. If you double the frequency of the voltage source, the effect on the circuit is to

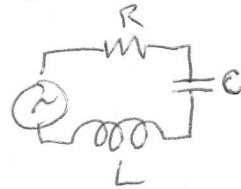- a) double the capacitive reactance. \times
- b) double the inductive reactance. \checkmark
- c) leave the total reactance unchanged. \times
- d) halve the inductive reactance. \times
- e) halve the impedance. \times
- f) none of the above.



$$X_C = \frac{1}{\omega C}$$

$$X_C' = \frac{1}{2} X_C$$

$$X_L = \omega L$$

$$X_L' = 2X_L$$

$$Z = (R^2 + (X_L - X_C)^2)^{1/2}$$

$$X = X_L - X_C$$

5) [4PTS] The more rapidly a magnet moves away from a copper ring, the

- a) lower the induced current in the ring.
- b) greater the inductance of the ring.
- c) the lower the inductance of the ring.
- d) greater the induced current in the ring
- e) none of the above

$\frac{d\Phi_m}{dt}$ increases so V_{emf} increases

$V = IR$ so current increases

6) [4PT] Two very long wires, 60 cm apart, are hung parallel to each other. Current flows down each wire in opposite directions. Wire C has a current of $\frac{1}{4}$ Amps and wire B has a current of $\frac{1}{2}$ Amp.



- a) The two wires are attracted $F_C = \frac{1}{4}F_B$
- b) The two wires are attracted $F_C = \frac{1}{2}F_B$
- c) The two wires are attracted $F_C = F_B$
- d) The two wires are repelled $F_C = F_B$
- e) The two wires are repelled $F_C = 2F_B$
- f) The two wires are repelled $F_C = 4F_B$

We now $\vec{F}_C = -\vec{F}_B$


$$\vec{F} = q\vec{v} \times \vec{B}$$

The force on each wire is towards the outside

Force on wire C

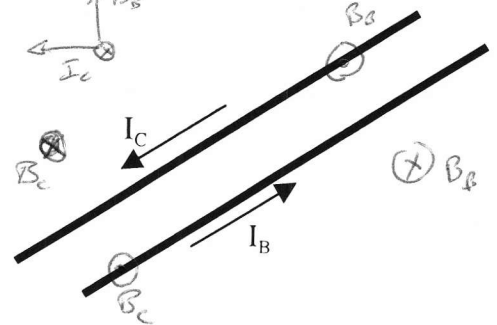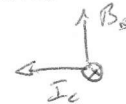

Force on wire B

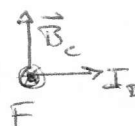


- 7) [4 PTS] A closed loop is placed next to a wire. The wire carries a constant current of 50 mA. The loop is started rotating next to the wire with a constant angular velocity ω .
- There will be no induced current. \times
 - There is a constant induced current. \times
 - There will only be an induced current if ω is along the z-axis. \times
 - There is an oscillating induced current if ω is along the y-axis. \checkmark
 - None of the above \times

\vec{B} wraps around the wire and is constant

$\frac{d\Phi_{int}}{dt} = -V_{emf}$ $\Phi_{int} = \int \vec{B} \cdot d\vec{A}$

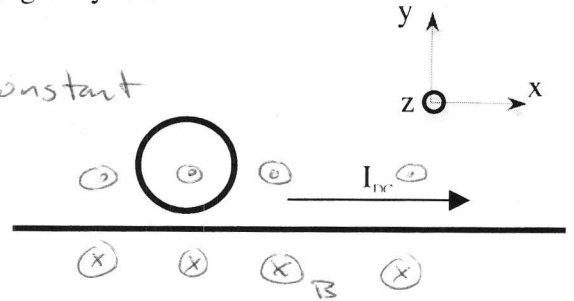while \vec{B} is constant the area will change if the loop rotates around \hat{y} or \hat{x}



- 8) [15 PT] You have connected an inductor ($L=8.0$ mH), a capacitor ($C=80\mu\text{F}$) and resistor ($R=100\ \Omega$) in series. You connect your LCR circuit to a function generator that is producing a sinusoidal voltage signal with a peak to peak amplitude of 16 volts at a frequency of 880 Hz.
- What is the resonant frequency for this circuit?
 - Write the equation for the voltage across the function generator if $V_o(t=0 \text{ sec}) = 0 \text{ V}$.
 - What is the impedance of this LCR circuit when it is at resonance?
 - What is the RMS current passing through the resistor?
 - What is the voltage as a function of time across the capacitor?


Useful mathematical relationships:

$$\sin^2(\theta) + \cos^2(\theta) = 1 \quad \text{and} \quad \sin(2\theta) = 2 \sin(\theta) \cos(\theta)$$

$$\cos(2\theta) = \cos^2(\theta) - \sin^2(\theta) = 2 \cos^2(\theta) - 1 = 1 - 2 \sin^2(\theta)$$

$$\int_b^c \frac{a}{x} = a \ln x \Big|_b^c = a[\ln c - \ln b] = a \ln\left(\frac{c}{b}\right)$$

8

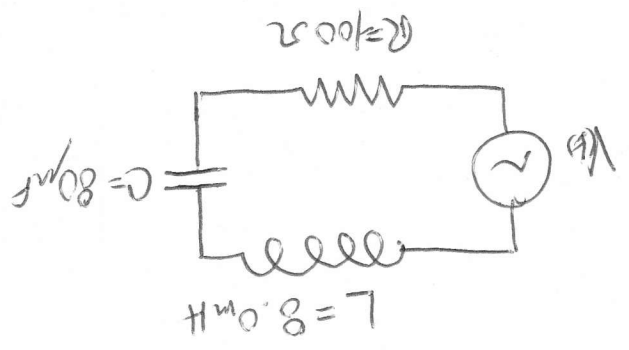

(a)

$$\omega_0 = \frac{1}{\sqrt{LC}} = 1250 \text{ rad/sec}$$

$$\omega_0 = 2\pi f_0 \text{ so } f_0 = \frac{\omega_0}{2\pi} = 199 \text{ Hz}$$

(b)

$$V_0(t) = V_p \sin(\omega t + \delta)$$

$$V_0(t=0) = V_p \sin(\omega \cdot 0 + \delta)$$

so $\delta = 0$ so sine function is ϕ

$$V_0(t) = 8 \sin(2\pi 880 \text{ Hz } t) \text{ Volts}$$

$$= 8 \sin(5530 t) \text{ Volts}$$

(c)

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

when $\omega = \omega_0$ $X_L = X_C$

$Z = R$ when $\omega = \omega_0$ (at resonance)

(d)

$$V_R = IR$$

$$I = \frac{V_0}{Z}$$

$$V_0 = \frac{V_R}{R} = 5.66 \text{ V}_{rms}$$

$$Z = \sqrt{100^2 + (5530 \cdot 8 \text{ mH} - \frac{1}{5530 \cdot 80 \mu\text{F}})^2} = 108 \Omega$$

$$I_{rms} = \frac{5.66 \text{ V}_{rms}}{108 \Omega} = 0.052 \text{ A}_{rms}$$

$$= 108 \Omega$$

$$\delta = 0$$

$$\omega = 2\pi f$$

$$V_p = 16 \text{ V} / \sqrt{2} = 8 \text{ V}$$

$$f = 880 \text{ Hz}$$

$$V(t) = V_p \sin(\omega t + \delta)$$

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

$$\textcircled{e} \quad V_c(t) = ?$$

$$V_c(t) = \frac{-V_p}{\omega C Z} \cos(\omega t + \delta)$$

$$V_c(t) = -0.17 \cos(5530 t + 23^\circ) \text{ Volts}$$

$$Q = CV_c$$

$$I = C \frac{dV_c}{dt} \text{ so } V_c(t) = \frac{1}{C} \int I dt$$

so need to find $I(t)$

$$I(t) = \frac{V_o(t)}{Z}$$

$$\therefore I_p = \frac{V_p}{|Z|} = 0.074 \text{ Amps}$$

$$\delta = \tan^{-1}\left(\frac{X}{R}\right) = \tan^{-1}\left(\frac{42}{100}\right) = 22.8^\circ$$

$$X = X_L - X_C = 42 \Omega$$

$$V_c(t) = \frac{1}{C} \int 0.074 \sin(\omega t + 22.8^\circ) dt$$

$$= \frac{-1}{\omega C} \cdot 0.074 \cdot \cos(\omega t + 22.8^\circ)$$

↑ voltage