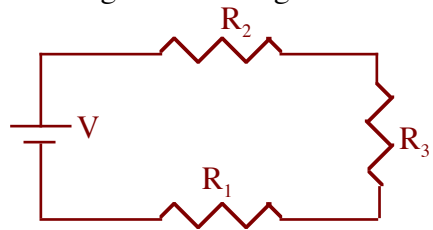


Exam 2 – Capacitance, Circuits and Magnetism

March 5, 2009

This is a closed book examination. However, you may use a 8.5" x 11" sheet of paper with your own notes during this exam. There is extra scratch paper available. Please explain your answers. Your explanation is worth 3/4 of the points on multiple-choice questions.


- 1) [4 PTS] What is the net force on a neutron ($q = 0$) with velocity $\vec{v} = 50 \text{ m/s } \hat{i}$ traveling through a region of space with $\vec{E} = 40 \text{ V/m } \hat{j}$ and $\vec{B} = 1.5 \text{ T } \hat{k}$?
- 2) [4 PTS] Two light bulbs (A and B) are connected in series. Bulb A is twice as bright as bulb B. What must be true?
- $2R_B = R_A$
 - $\sqrt{2} I_B = I_A$
 - Bulb A receives the current from the battery first (closest to positive terminal)
 - Bulb B receives the current from the battery first (closest to positive terminal)
 - $2R_A = R_B$
 - $\sqrt{2} I_A = I_B$
- 3) [4 PTS] You connect three resistors to a battery as shown in the diagram to the right. Which resistor has the most current flowing through it?
- R_1
 - R_2
 - R_3
 - Which ever one has the smallest resistance.
 - Which ever one has the largest resistance.
 - The current is the same through all of them.



- 5) [4 PTS] The light bulbs in the circuit to the right have different resistances, $R_1 = 2R_2 = 4R_3$. Which bulb is brightest (uses the most power)?
- R_1
 - R_2
 - R_3
 - All the light bulbs are of equal brightness since they have the same voltage across them.

- 6) [4 PTS] A charged particle is moving in a uniform magnetic field (coming out of the page) as shown in the figure to the right. What type of particle would follow the path indicated?

- Proton
- Neutron
- Electron
- Photon

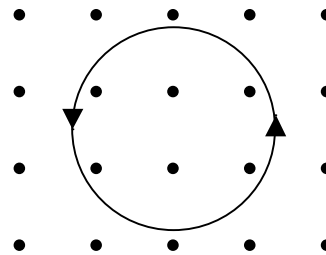

- 7) [12 PTS] A charged capacitor ($C=3.2 \text{ mF}$) is connected to a resistive load ($R=100 \Omega$) at time $t=0\text{s}$. The capacitor is initially charged to 5.1 Volts.
- What is the time constant for this circuit?
 - What is the initial energy stored in the capacitor?
 - How much energy is left in the capacitor at time $t=\tau$?
 - What is the power used by the load as a function of time?

- 8) [12 PTS] Solve for the unknown source voltage, the current through resistor R_1 and the power used by resistor R_5 in the diagram below. The current through R_2 is 1,666 mA while $R_1 = 8 \Omega$, $R_2 = R_5 = 2 \Omega$ and $R_3 = 4 \Omega$.

