

**Exam 2 – Capacitance, Circuits and Magnetism**


March 11, 2010

This is a closed book examination but during the exam you may refer to a 4"x6" note card with words of wisdom you have written on it. There is extra scratch paper available. Please explain your answers. Your explanation is worth 3/4 of the points on all questions.

A general reminder about problem solving:


- |   |   |
|---|---|
| <ul style="list-style-type: none"> <li>• <b>Focus</b> <ul style="list-style-type: none"> <li>○ Draw a picture of the problem</li> <li>○ What is the question? What do you want to know?</li> <li>○ List known and unknown quantities</li> <li>○ List assumptions</li> </ul> </li> <li>• <b>Physics</b> <ul style="list-style-type: none"> <li>○ Determine approach – What physics principles will you use?</li> <li>○ Pick a coordinate system</li> <li>○ Simplify picture to a schematic (if needed)</li> </ul> </li> <li>• <b>Plan</b> <ul style="list-style-type: none"> <li>○ Divide problem into sub-problems</li> </ul> </li> </ul> | <ul style="list-style-type: none"> <li>○ Modify schematic and coordinate system (if needed)</li> <li>○ Write general equations</li> <li>• <b>Execute</b> <ul style="list-style-type: none"> <li>○ Write equations with variables</li> <li>○ Do you have sufficient equations to determine your unknowns?</li> <li>○ Simplify and solve</li> </ul> </li> <li>• <b>Evaluate</b> <ul style="list-style-type: none"> <li>○ Check units</li> <li>○ Why is answer reasonable?</li> <li>○ Check limiting cases!</li> </ul> </li> <li>• <b>Show All Your Work!</b></li> </ul> |
|---|---|

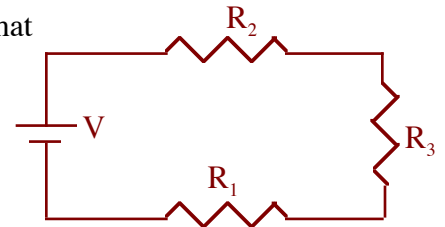- 1) [4 PTS] You connect three light bulbs (resistors) to a battery as shown in the diagram to the right. If the light bulb labeled  $R_2$  is brightest, what must be true?
- $R_2$  has the largest resistance.
  - $R_2$  is first resistor so it has largest current through it.
  - $R_2$  has the smallest resistance.
  - $R_2$  has the smallest voltage drop.



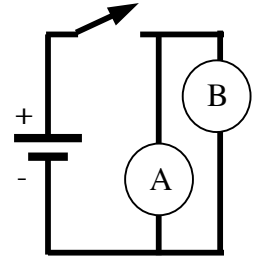- 2) [4 PTS] A current carrying wire is placed between the poles of a strong magnet. The magnetic field is in the  $-y$  direction and the wire is along the  $x$ -axis. If the wire is deflected in the  $+z$  direction what is the direction of the current?
- The current is traveling in the  $-x$  direction.
  - The current is traveling in the  $+x$  direction.
  - The current is not moving but there is a net negative charge on the wire.
  - The current is not moving but there is a net positive charge on the wire.

The next two problems involve the circuit to the right. A capacitor is placed at position B and a light bulb is placed at position A. Assume the voltage source can provide any current.



- 3) [4 PTS] The capacitor is initially uncharged. When the switch is closed what happens?
- The light bulb does not light.
  - The light bulb starts off dim and then gets brighter.
  - The light bulb turns on and is a constant brightness.
  - The light bulb starts off bright and then gets dimmer.
- 4) [4 PTS] After a long time the switch is then opened. What happens?
- Nothing. The light bulb was off and it stays off.
  - The light bulb starts off dim and then gets brighter.
  - Nothing. The light bulb turns on and stays on.
  - The light bulb starts off bright and then gets dimmer.
- 5) [4 PTS] You are measuring the voltage across a capacitor with a charge  $Q$  on it. How does the voltage change when you insert a dielectric with  $\kappa=2$  into the capacitor.
- The voltage decreases.
  - The voltage does not change.
  - The voltage increases.
- 6) [4 PTS] A parallel plate capacitor is charged and stores a total energy of  $U_i$ . You decide to increase the plate separation by 4 (i.e. they were separated by 1 mm and now they are separated by 4 mm). What is the new energy stored in the capacitor?
- $U_f = \frac{1}{2}U_i$
  - $U_f = \frac{1}{4}U_i$
  - $U_f = U_i$
  - $U_f = 2U_i$
  - $U_f = 4U_i$
  - $U_f = 16U_i$

- 7) [4 PTS] The radioactive decay of  $^{18}\text{F}$  produces a positron that is initially at rest in a vacuum chamber. The positron (a positively charged electron) is in the middle of a uniform magnetic field of magnitude 2 Teslas. The field is in the  $+z$  direction where the gravitational acceleration is in the  $-z$  direction. How does the positron move?
- The positron moves in a circle with an angular velocity vector in the  $+z$  direction.
  - The positron moves in the  $-z$  direction.
  - The positron moves in the  $+z$  direction.
  - The positron moves in a circle with an angular velocity vector in the  $-z$  direction.
- 8) [4 PTS] An electron moving in the  $+x$  direction enters a region of uniform magnetic field that is also oriented in the  $+x$  direction. In which direction does the electron feel a force?
- The  $+y$  direction.
  - The  $+z$  direction.
  - The  $-y$  direction.
  - The  $-z$  direction.
  - None of the above.
- 9) [4 PTS] For the circuit to the right the light bulb labeled  $R_3$  is the brightest and the light bulb labeled  $R_1$  is the dimmest. The circuit is now changed to resemble the circuit in question #1. How does the brightness of the light bulbs change? \_\_\_\_\_
- $R_2$  is now the brightest light bulb.
  - $R_3$  is still the brightest light bulb.
  - $R_1$  is now the brightest light bulb.
  - All the light bulbs are of equal brightness.

10) [24 PTS] You construct the circuit shown to the right with  $R_1 = 250\Omega$ ,  $R_2 = 750\Omega$ ,  $C_1 = 40\mu\text{F}$ ,  $C_2 = 10\mu\text{F}$  and  $V = 3\text{Volts}$ . The capacitors are initially uncharged. NOTE: When graphing  $V(t)$  and  $I(t)$  make sure to label both axis with actual values.

- What is the time constant for the entire circuit?
- Which resistor has the largest voltage drop across it?
- Which resistor has the largest current through it?
- Graph the voltage across  $C_2$  as a function of time.
- Graph the current through  $C_1$  as a function of time.
- Graph the current through  $R_1$  as a function of time.
- How long does it take  $C_1$  to charge to 2 volts?
- What is the charge on each capacitor at  $t = 75\text{ msec}$ ?

