

(+6)

Obtain a general solution:

(+1) Find P_{max} through R
 $P_{max} = I_{max}^2 R$
 $I_{max} = ?$


Most current flows through $5\Omega \equiv R$ when R_v is as large as possible ("current takes path of least resistance")

Thus $R_v = R_{vmax}$ (1)


Then $P_{max} = I_{max}^2 \cdot R$ (2)

So find $I_{max} = \frac{\Delta V_{max}}{R}$, $\Delta V_{max} = ?$ (3)

$\Delta V_{max} = ?$

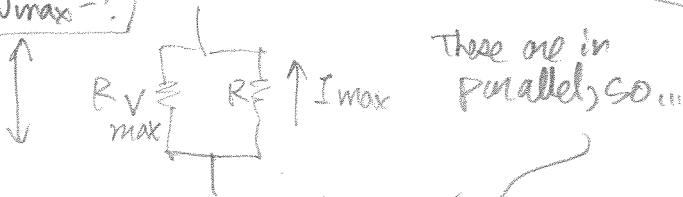

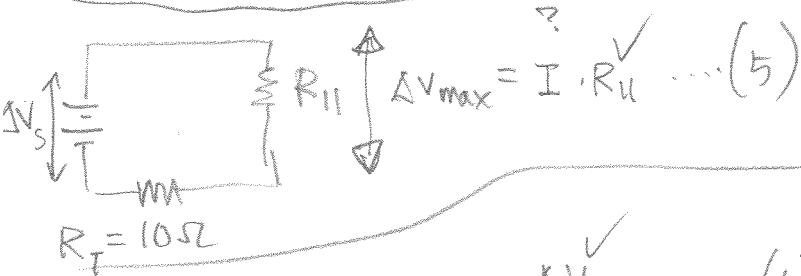$R_{11} = \frac{R_{vmax} \cdot R}{R_{vmax} + R}$ (4)



To find I , $I = \frac{\Delta V_s}{R_T + R_{11}}$ (6)

So $\Delta V_{max} = \frac{\Delta V_s}{R_T + R_{11}} \cdot R_{11}$ (7)

$I_{max} = \frac{\Delta V_{max}}{R}$ (8)

Check Units:

$\left[\frac{J}{s} \right] = \frac{\left(\frac{V}{\Omega} \cdot \Omega \right)^2}{\Omega} = \frac{V^2}{\Omega} = W$

(+2)

Check Limiting Cases:

Expect as $\Delta V_s \rightarrow \infty$, $P_{max} \rightarrow \infty$;

$\lim_{\Delta V_s \rightarrow \infty} \left(\frac{\Delta V_s \cdot R_{11}}{R_T + R_{11}} \right)^2 \cdot \frac{1}{R} \rightarrow \infty$, so it works

(+2)

Obtain a numeric solution:

(i.e. plug in the numbers)

$\Delta V_s = 115V$
 $R_T = 10\Omega$
 $R = 5\Omega$
 $R_{11} = \frac{5\Omega \cdot 20\Omega}{5\Omega + 20\Omega} = 4\Omega$
 $P_{max} = \frac{\left(\frac{115V}{10\Omega + 4\Omega} \cdot 4\Omega \right)^2}{5\Omega} = 216W$

Why is solution reasonable? Explain.

216W makes sense; 100W light bulb feels really hot! 216W makes sense for a toaster

General formula $R_{11} = \frac{R_{vmax} \cdot R}{R_{vmax} + R}$
 $P_{max} = \frac{\left(\frac{\Delta V_s}{R_T + R_{11}} \cdot R_{11} \right)^2}{R}$
 $\rightarrow P_{max} = I_{max}^2 \cdot R = \frac{\Delta V_{max}^2}{R}$